

嵌入式系统结构与课程实验

# 实验报告 9

ALU (Arithmetic and Logic Unit) Design and ALU Pipeline



## Content

|   |    |
|---|----|
| 1. Target .....                                       | 1  |
| 2. Arithmetic and Logic Unit .....                    | 1  |
| 2.1 Designing .....                                   | 1  |
| 2.2 Simulation .....                                  | 1  |
| 2.3 Synthesization and RTL diagram .....              | 3  |
| 2.4 Design Summary .....                              | 3  |
| 3. ALU Pipeline Example .....                         | 5  |
| 3.1 Design .....                                      | 5  |
| 3.2 Simulation .....                                  | 5  |
| 2.3 Synthesization and RTL diagram .....              | 6  |
| 2.4 Design Summary .....                              | 6  |
| Afterthought .....                                    | 8  |
| Appendix 1: Attachment List.....                      | 9  |
| Appendix 2: ALU Operation List .....                  | 10 |
| Appendix 3: RTL Diagram.....                          | 11 |
| Appendix 4: Timing Constraints Report .....           | 12 |
| Appendix 5: RTL Diagram of ALU Pipeline Example ..... | 19 |



# 1. Target

- Design an ALU (arithmetic logic unit)
- Further understand and use timing/area/power report to optimize the design

## 2. Arithmetic and Logic Unit

### 2.1 Designing

The most important step is to design the available operation list. By following the operation list, actual ALU implementation is much easier.

Since the available operations of ALU are directly affected what the CPU can execute, and the optimization of the ALU is related to the CPU requirements, I have to wait until our CPU design instruction comes out. I'm sorry for the latency of my assignment, but I really want to implement a complete and optimal ALU.

The available ALU operations are as followed.

*(See Appendix 2: ALU Operation List)*

In accord to special CPU design for optimization, only a half of the CPU's instructions are necessary being an individual operation within the ALU, thus a 5-bit-instruction CPU requires only a 4-bit-opcode ALU. And these operation codes are allocated after 10000 of the instruction code table.

### 2.2 Simulation

Test is based on texture test bench, and the result is as followed.

```
TEST 01 : (1)0000 [ADD]
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF
0000:f002:0fff:0    :0001:1    :0    :0

TEST 02 : (1)0001 [ADDI]
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF
0001:102c:59ff:0    :6a2b:0    :0    :0

TEST 03 : (1)0010 [ADDC]
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF
0010:2008:0108:1    :2111:0    :0    :0
```

TEST 04 : (1)0011 [SUB]  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
0011:1000:08ff:0 :0701:0 :0 :0

TEST 05 : (1)0100 [SUBI]  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
0100:0001:1000:0 :f001:0 :0 :1

TEST 06 : (1)0101 [SUBC]  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
0101:1000:0fff:1 :0000:0 :1 :0

TEST 07 : (1)0110 [INC]  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
0110:0fff:0000:0 :1000:0 :0 :0

TEST 08 : (1)0111 [CMP] - less  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
0111:21fc:2f56:0 :0000:0 :1 :0

TEST 09 : (1)0111 [CMP] - equal  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
0111:64ff:64ff:0 :0000:0 :1 :0

TEST 10 : (1)0111 [CMP] - larger  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
0111:b9a8:975f:0 :0000:0 :1 :0

TEST 11 : (1)1000 [TRAN]  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
1000:56fc:0000:0 :56fc:0 :0 :0

TEST 12 : (1)1001 [XOR]  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
1001:ff0f:f0fa:0 :0ff5:0 :0 :0

TEST 13 : (1)1010 [AND]  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
1010:f00f:ff0a:0 :f00a:0 :0 :0

TEST 14 : (1)1011 [OR]  
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF  
1011:f00f:ff0a:0 :ff0f:0 :0 :0

```

TEST 15 : (1)1100 [SLL]
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF
1100:f0f0:0004:0 :0f00:1 :0 :0

TEST 16 : (1)1101 [SLA]
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF
1101:0f0f:0004:0 :f0f0:0 :0 :0

TEST 17 : (1)1110 [SRL]
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF
1110:f000:0004:0 :0f00:0 :0 :0

TEST 18 : (1)1111 [SRA]
OPC :IN1 :IN2 :ICF :OUT :OCF :OZF :ONF
1111:f0ff:0004:0 :ff0f:1 :0 :0

```

## 2.3 Synthesization and RTL diagram

After Synthesization RTL diagram of the design is generated.

The RTL diagram of the core module, the ALU module, generated from Synthesization is as below.

*(See Appendix 3: RTL Diagram)*

## 2.4 Design Summary

### Device utilization summary:

```

Slice Logic Utilization:
Number of Slice LUTs:                246 out of 9112 2%
Number used as Logic:                246 out of 9112 2%

Slice Logic Distribution:
Number of LUT Flip Flop pairs used:  246
Number with an unused Flip Flop:     246 out of 246 100%
Number with an unused LUT:           0 out of 246 0%
Number of fully used LUT-FF pairs:    0 out of 246 0%
Number of unique control sets:        0

IO Utilization:
Number of IOs:                        56
Number of bonded IOBs:                56 out of 232 24%

Specific Feature Utilization:

```

**Timing Constraints:**

The timing constraints report is as follow.

*(See Appendix 4: Timing Constraints Report)*

**Power Report:**


| On-Chip Power Summary |            |      |           |                 |    |
|-----------------------|------------|------|-----------|-----------------|----|
| On-Chip               | Power (mW) | Used | Available | Utilization (%) |    |
| Clocks                | 0.00       | 0    | ---       | ---             |    |
| Logic                 | 0.00       | 235  | 9112      |                 | 3  |
| Signals               | 0.00       | 274  | ---       | ---             |    |
| IOs                   | 0.00       | 56   | 232       |                 | 24 |
| Quiescent             | 14.84      |      |           |                 |    |
| Total                 | 14.84      |      |           |                 |    |



## 3. ALU Pipeline Example
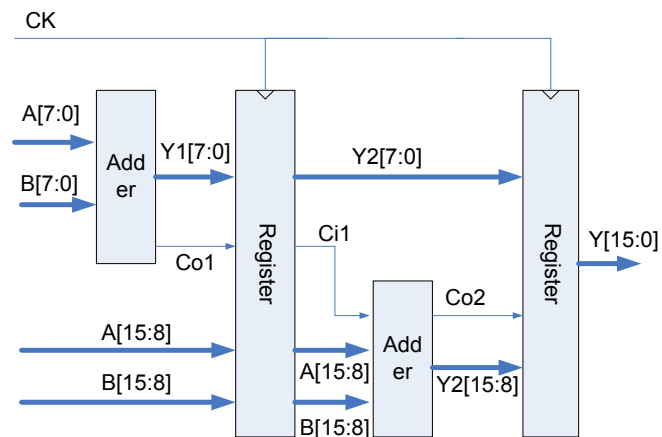
### 3.1 Design

In pipeline ALU design, the implementation is not complete, rather only addition operation is implemented as an example. The design follows the following architecture.



There are 2 stages of pipeline in this design, with each computing 8 bits of the inputs.

### 3.2 Simulation

The simulation involves 4 clock trigger pulses, and inputs of each pulse are as followed.

| Clock# | Input |      |       |
|--------|-------|------|-------|
|        | IN1   | IN2  | Carry |
| 1      | 01FF  | 0102 | 0     |
| 2      | 1F05  | 0100 | 0     |
| 3      | 0     | 0    | 0     |
| 4      | 0     | 0    | 0     |

The result of simulation is as followed.

```
Pipeline ALU example testing
IN1 :IN2 :ICF ::OUT :OCF :OZF :ONF
01ff:0102:0  ::0000:0  :x  :x
1f05:0100:0  ::0000:0  :x  :x
0000:0000:0  ::0301:0  :0  :0
0000:0000:0  ::2005:0  :0  :0
0000:0000:0  ::0000:0  :0  :0
```

## 2.3 Synthesization and RTL diagram

After Synthesization RTL diagram of the design is generated.

The RTL diagram of the core module, the ALUP2 module, generated from Synthesization is as below.

(See Appendix 5: RTL Diagram of ALU Pipeline Example)

## 2.4 Design Summary

### Device utilization summary:

|                                     |    |        |       |     |
|-------------------------------------|----|--------|-------|-----|
| Slice Logic Utilization:            |    |        |       |     |
| Number of Slice Registers:          | 36 | out of | 18224 | 0%  |
| Number of Slice LUTs:               | 27 | out of | 9112  | 0%  |
| Number used as Logic:               | 19 | out of | 9112  | 0%  |
| Number used as Memory:              | 8  | out of | 2176  | 0%  |
| Number used as SRL:                 | 8  |        |       |     |
| Slice Logic Distribution:           |    |        |       |     |
| Number of LUT Flip Flop pairs used: | 46 |        |       |     |
| Number with an unused Flip Flop:    | 10 | out of | 46    | 21% |
| Number with an unused LUT:          | 19 | out of | 46    | 41% |
| Number of fully used LUT-FF pairs:  | 17 | out of | 46    | 36% |
| Number of unique control sets:      | 2  |        |       |     |
| IO Utilization:                     |    |        |       |     |
| Number of IOs:                      | 53 |        |       |     |
| Number of bonded IOBs:              | 53 | out of | 232   | 22% |
| Specific Feature Utilization:       |    |        |       |     |
| Number of BUFG/BUFGCTRLs:           | 1  | out of | 16    | 6%  |

### Timing Report:

The timing report is as follow.

Clock to Setup on destination clock CLK

|              | Src:Rise  | Src:Fall  | Src:Rise  | Src:Fall  |
|--------------|-----------|-----------|-----------|-----------|
| Source Clock | Dest:Rise | Dest:Fall | Dest:Fall | Dest:Fall |
| CLK          | 2.863     |           |           |           |

**Power Report:**

| On-Chip Power Summary |            |      |           |                 |    |
|-----------------------|------------|------|-----------|-----------------|----|
| On-Chip               | Power (mW) | Used | Available | Utilization (%) |    |
| Clocks                | 0.01       | 1    | ---       | ---             |    |
| Logic                 | 0.00       | 24   | 9112      |                 | 0  |
| Signals               | 0.00       | 82   | ---       | ---             |    |
| IOs                   | 0.00       | 53   | 232       |                 | 23 |
| Quiescent             | 14.84      |      |           |                 |    |
| Total                 | 14.86      |      |           |                 |    |

# Afterthought

CPU design is a big topic: a lot of technologies, theories, techniques and knowledge are required. Since the CPU is exact a highly coupling module, one has to think hard to optimize the design until the final product comes out. Hence, I am half exciting and half worrying about this assignment.

As I once thought, merely the design of ALU, a component of the CPU, costs me a lot of time.

To build an experimental, or says example, ALU is easy with the guidance from our teacher. However, what I want to build is an ALU fit and optimized for the later CPU design, which means these two designs is highly coupling but quite optimized that they seem to be exactly one piece.

So I had to wait for the final assignment of our CPU design, before I could start to build my ALU. What's more, I consider this project a real one, so I pushed it as a currently not visible open source project. What I mean by invisible is because I do not want my homework be copied, so I just hide it from the public currently, but later I will make it visible. A lot of documentation and details are required in my design. So I design the both the operation tables of CPU and ALU together, actually. To apply a lot of tricks in the design actually cost a majority of my time on this project, for example, the order of operation code allocation.

I wanted to optimize this design as far as possible, but the payment is time. I am so sorry that I submit my homework so late. But the outcome is not so bad, because merely all my initial expectations finally come true in my design.

David Qiu (邱迪聪)

2013.12.24

# Appendix 1: Attachment List

## 1. ALU

\ ALU.v

\ ALU\_test01.v

## 2. ALU pipeline example

\ ALUP2\_example.v


\ ALUP2\_example\_test01.v

X.v files are primary code files; X\_test.v files are test files.

# Appendix 2: ALU Operation List

| Arithmetic and Logic Unit Operation List |          |         |         |             |         |              |        |                          |  |
|--|----------|---------|---------|-------------|---------|--------------|--------|--------------------------|--|
| Category                                 | Mnemonic | Input1  | Input2  | Input Flags | Output  | Output Flags | Opcode | Full Name                | Operation  |
| Arithmetic                               | ADD      | bit[16] | bit[16] | /           | bit[16] | CF, ZF, NF   | 10000  | ADD                      | Input1+Input2 -> Output                          |
|  | ADDI     | bit[16] | bit[16] | /           | bit[16] | CF, ZF, NF   | 10001  | ADD IMMEDIATE            | Input1+Input2 -> Output                          |
|  | ADDC     | bit[16] | bit[16] | CF          | bit[16] | CF, ZF, NF   | 10010  | ADD CARRY                | Input1+Input2+Carry -> Output                    |
|  | SUB      | bit[16] | bit[16] | /           | bit[16] | CF, ZF, NF   | 10011  | SUBTRACT                 | Input1-Input2 -> Output                          |
|  | SUBI     | bit[16] | bit[16] | /           | bit[16] | CF, ZF, NF   | 10100  | SUBTRACT IMMEDIATE       | Input1-Input2 -> Output                          |
|  | SUBC     | bit[16] | bit[16] | CF          | bit[16] | CF, ZF, NF   | 10101  | SUBTRACT CARRY           | Input1-Input2-Borrow -> Output                   |
|  | INC      | bit[16] | /       | /           | bit[16] | CF, ZF, NF   | 10110  | INCREASE                 | Input1+1 -> Output                               |
|  | CMP      | bit[16] | bit[16] | /           | 0       | CF, ZF, NF   | 10111  | COMPARE                  | Input1-Input2                                    |
| Special                                  | TRAN     | bit[16] | /       | /           | bit[16] | ZF           | 11000  | TRANSFER                 | Input1 -> Output                                 |
|  | XOR      | bit[16] | bit[16] | /           | bit[16] | ZF           | 11001  | EXCLUSIVE OR             | Input1 XOR Input2 -> Output                      |
| Logic                                    | AND      | bit[16] | bit[16] | /           | bit[16] | ZF           | 11010  | AND                      | Input1 AND Input2 -> Output                      |
|  | OR       | bit[16] | bit[16] | /           | bit[16] | ZF           | 11011  | OR                       | Input1 OR Input2 -> Output                       |
| Shift                                    | SLL      | bit[16] | bit[16] | /           | bit[16] | CF, ZF       | 11100  | SHIFT LEFT LOGICAL       | {CF, Input1, 0} << Input2[3:0] -> Output         |
|  | SLLA     | bit[16] | bit[16] | /           | bit[16] | CF, ZF       | 11101  | SHIFT LEFT ARITHMETICAL  | {CF, Input1, 0} << Input2[3:0] -> Output         |
|  | SRL      | bit[16] | bit[16] | /           | bit[16] | CF, ZF       | 11110  | SHIFT RIGHT LOGICAL      | {0, Input1, CF} >> Input2[3:0] -> Output         |
|  | SRA      | bit[16] | bit[16] | /           | bit[16] | CF, ZF       | 11111  | SHIFT RIGHT ARITHMETICAL | {Input1[0], Input1, CF} >> Input2[3:0] -> Output |

## Appendix 3: RTL Diagram

 

## Appendix 4: Timing Constraints Report

All values displayed in nanoseconds (ns)

Pad to Pad

| Source Pad | Destination Pad | Delay  |
|------------|-----------------|--------|
| ICF        | OCF             | 12.463 |
| ICF        | ONF             | 12.773 |
| ICF        | OUT<0>          | 12.032 |
| ICF        | OUT<1>          | 12.327 |
| ICF        | OUT<2>          | 11.515 |
| ICF        | OUT<3>          | 12.177 |
| ICF        | OUT<4>          | 13.068 |
| ICF        | OUT<5>          | 11.950 |
| ICF        | OUT<6>          | 12.756 |
| ICF        | OUT<7>          | 12.149 |
| ICF        | OUT<8>          | 12.227 |
| ICF        | OUT<9>          | 13.008 |
| ICF        | OUT<10>         | 12.944 |
| ICF        | OUT<11>         | 12.878 |
| ICF        | OUT<12>         | 13.428 |
| ICF        | OUT<13>         | 13.128 |
| ICF        | OUT<14>         | 12.531 |
| ICF        | OUT<15>         | 13.458 |
| ICF        | OZF             | 15.103 |
| IN1<0>     | OCF             | 13.174 |
| IN1<0>     | ONF             | 14.526 |
| IN1<0>     | OUT<0>          | 12.970 |
| IN1<0>     | OUT<1>          | 14.613 |
| IN1<0>     | OUT<2>          | 13.583 |
| IN1<0>     | OUT<3>          | 15.084 |
| IN1<0>     | OUT<4>          | 14.173 |
| IN1<0>     | OUT<5>          | 13.683 |
| IN1<0>     | OUT<6>          | 14.047 |
| IN1<0>     | OUT<7>          | 13.692 |
| IN1<0>     | OUT<8>          | 14.116 |
| IN1<0>     | OUT<9>          | 15.145 |
| IN1<0>     | OUT<10>         | 14.369 |
| IN1<0>     | OUT<11>         | 13.902 |
| IN1<0>     | OUT<12>         | 14.734 |
| IN1<0>     | OUT<13>         | 13.849 |

|        |         |        |
|--------|---------|--------|
| IN1<0> | OUT<14> | 13.242 |
| IN1<0> | OUT<15> | 15.059 |
| IN1<0> | OZF     | 17.591 |
| IN1<1> | OCF     | 13.650 |
| IN1<1> | ONF     | 14.651 |
| IN1<1> | OUT<0>  | 11.071 |
| IN1<1> | OUT<1>  | 14.689 |
| IN1<1> | OUT<2>  | 13.659 |
| IN1<1> | OUT<3>  | 15.160 |
| IN1<1> | OUT<4>  | 14.249 |
| IN1<1> | OUT<5>  | 13.759 |
| IN1<1> | OUT<6>  | 14.123 |
| IN1<1> | OUT<7>  | 13.768 |
| IN1<1> | OUT<8>  | 14.192 |
| IN1<1> | OUT<9>  | 15.221 |
| IN1<1> | OUT<10> | 14.445 |
| IN1<1> | OUT<11> | 14.050 |
| IN1<1> | OUT<12> | 14.810 |
| IN1<1> | OUT<13> | 14.315 |
| IN1<1> | OUT<14> | 13.718 |
| IN1<1> | OUT<15> | 15.184 |
| IN1<1> | OZF     | 17.667 |
| IN1<2> | OCF     | 13.174 |
| IN1<2> | ONF     | 13.912 |
| IN1<2> | OUT<0>  | 11.083 |
| IN1<2> | OUT<1>  | 10.237 |
| IN1<2> | OUT<2>  | 12.488 |
| IN1<2> | OUT<3>  | 13.985 |
| IN1<2> | OUT<4>  | 13.305 |
| IN1<2> | OUT<5>  | 12.602 |
| IN1<2> | OUT<6>  | 13.272 |
| IN1<2> | OUT<7>  | 12.917 |
| IN1<2> | OUT<8>  | 13.364 |
| IN1<2> | OUT<9>  | 14.393 |
| IN1<2> | OUT<10> | 13.636 |
| IN1<2> | OUT<11> | 13.574 |
| IN1<2> | OUT<12> | 14.139 |
| IN1<2> | OUT<13> | 13.839 |
| IN1<2> | OUT<14> | 13.242 |
| IN1<2> | OUT<15> | 14.445 |
| IN1<2> | OZF     | 16.492 |



|        |         |  |        |        |         |  |        |
|--------|---------|--|--------|--------|---------|--|--------|
| IN1<3> | OCF     |  | 12.946 | IN1<5> | OUT<4>  |  | 11.566 |
| IN1<3> | ONF     |  | 14.101 | IN1<5> | OUT<5>  |  | 13.357 |
| IN1<3> | OUT<0>  |  | 10.740 | IN1<5> | OUT<6>  |  | 13.971 |
| IN1<3> | OUT<1>  |  | 10.619 | IN1<5> | OUT<7>  |  | 13.616 |
| IN1<3> | OUT<2>  |  | 12.057 | IN1<5> | OUT<8>  |  | 14.094 |
| IN1<3> | OUT<3>  |  | 14.027 | IN1<5> | OUT<9>  |  | 15.123 |
| IN1<3> | OUT<4>  |  | 13.214 | IN1<5> | OUT<10> |  | 14.347 |
| IN1<3> | OUT<5>  |  | 12.710 | IN1<5> | OUT<11> |  | 14.249 |
| IN1<3> | OUT<6>  |  | 13.461 | IN1<5> | OUT<12> |  | 14.814 |
| IN1<3> | OUT<7>  |  | 13.106 | IN1<5> | OUT<13> |  | 14.514 |
| IN1<3> | OUT<8>  |  | 13.553 | IN1<5> | OUT<14> |  | 13.917 |
| IN1<3> | OUT<9>  |  | 14.582 | IN1<5> | OUT<15> |  | 15.177 |
| IN1<3> | OUT<10> |  | 13.806 | IN1<5> | OZF     |  | 16.822 |
| IN1<3> | OUT<11> |  | 13.346 | IN1<6> | OCF     |  | 12.913 |
| IN1<3> | OUT<12> |  | 14.171 | IN1<6> | ONF     |  | 14.698 |
| IN1<3> | OUT<13> |  | 13.611 | IN1<6> | OUT<0>  |  | 10.869 |
| IN1<3> | OUT<14> |  | 13.014 | IN1<6> | OUT<1>  |  | 9.863  |
| IN1<3> | OUT<15> |  | 14.634 | IN1<6> | OUT<2>  |  | 12.275 |
| IN1<3> | OZF     |  | 16.534 | IN1<6> | OUT<3>  |  | 10.419 |
| IN1<4> | OCF     |  | 13.482 | IN1<6> | OUT<4>  |  | 11.406 |
| IN1<4> | ONF     |  | 14.339 | IN1<6> | OUT<5>  |  | 12.916 |
| IN1<4> | OUT<0>  |  | 10.801 | IN1<6> | OUT<6>  |  | 14.004 |
| IN1<4> | OUT<1>  |  | 10.438 | IN1<6> | OUT<7>  |  | 13.649 |
| IN1<4> | OUT<2>  |  | 11.993 | IN1<6> | OUT<8>  |  | 14.120 |
| IN1<4> | OUT<3>  |  | 10.861 | IN1<6> | OUT<9>  |  | 15.149 |
| IN1<4> | OUT<4>  |  | 13.468 | IN1<6> | OUT<10> |  | 14.373 |
| IN1<4> | OUT<5>  |  | 12.809 | IN1<6> | OUT<11> |  | 13.906 |
| IN1<4> | OUT<6>  |  | 13.665 | IN1<6> | OUT<12> |  | 14.738 |
| IN1<4> | OUT<7>  |  | 13.310 | IN1<6> | OUT<13> |  | 13.853 |
| IN1<4> | OUT<8>  |  | 13.788 | IN1<6> | OUT<14> |  | 13.218 |
| IN1<4> | OUT<9>  |  | 14.817 | IN1<6> | OUT<15> |  | 15.231 |
| IN1<4> | OUT<10> |  | 14.041 | IN1<6> | OZF     |  | 16.876 |
| IN1<4> | OUT<11> |  | 13.882 | IN1<7> | OCF     |  | 12.653 |
| IN1<4> | OUT<12> |  | 14.447 | IN1<7> | ONF     |  | 14.528 |
| IN1<4> | OUT<13> |  | 14.147 | IN1<7> | OUT<0>  |  | 10.831 |
| IN1<4> | OUT<14> |  | 13.550 | IN1<7> | OUT<1>  |  | 10.460 |
| IN1<4> | OUT<15> |  | 14.872 | IN1<7> | OUT<2>  |  | 12.345 |
| IN1<4> | OZF     |  | 16.517 | IN1<7> | OUT<3>  |  | 10.383 |
| IN1<5> | OCF     |  | 13.849 | IN1<7> | OUT<4>  |  | 11.368 |
| IN1<5> | ONF     |  | 14.644 | IN1<7> | OUT<5>  |  | 13.513 |
| IN1<5> | OUT<0>  |  | 11.029 | IN1<7> | OUT<6>  |  | 11.976 |
| IN1<5> | OUT<1>  |  | 10.304 | IN1<7> | OUT<7>  |  | 13.438 |
| IN1<5> | OUT<2>  |  | 12.331 | IN1<7> | OUT<8>  |  | 13.938 |
| IN1<5> | OUT<3>  |  | 10.703 | IN1<7> | OUT<9>  |  | 14.967 |

|        |         |         |         |         |         |
|--------|---------|---------|---------|---------|---------|
| IN1<7> | OUT<10> | 14. 191 | IN1<9>  | OZF     | 16. 618 |
| IN1<7> | OUT<11> | 13. 724 | IN1<10> | OCF     | 12. 820 |
| IN1<7> | OUT<12> | 14. 556 | IN1<10> | ONF     | 14. 193 |
| IN1<7> | OUT<13> | 13. 671 | IN1<10> | OUT<0>  | 10. 228 |
| IN1<7> | OUT<14> | 13. 048 | IN1<10> | OUT<1>  | 10. 178 |
| IN1<7> | OUT<15> | 15. 061 | IN1<10> | OUT<2>  | 12. 110 |
| IN1<7> | OZF     | 16. 706 | IN1<10> | OUT<3>  | 10. 750 |
| IN1<8> | OCF     | 12. 962 | IN1<10> | OUT<4>  | 10. 479 |
| IN1<8> | ONF     | 14. 640 | IN1<10> | OUT<5>  | 11. 554 |
| IN1<8> | OUT<0>  | 10. 193 | IN1<10> | OUT<6>  | 11. 869 |
| IN1<8> | OUT<1>  | 10. 061 | IN1<10> | OUT<7>  | 11. 901 |
| IN1<8> | OUT<2>  | 11. 794 | IN1<10> | OUT<8>  | 10. 688 |
| IN1<8> | OUT<3>  | 10. 337 | IN1<10> | OUT<9>  | 11. 599 |
| IN1<8> | OUT<4>  | 10. 444 | IN1<10> | OUT<10> | 13. 412 |
| IN1<8> | OUT<5>  | 13. 114 | IN1<10> | OUT<11> | 12. 982 |
| IN1<8> | OUT<6>  | 11. 425 | IN1<10> | OUT<12> | 14. 172 |
| IN1<8> | OUT<7>  | 11. 488 | IN1<10> | OUT<13> | 13. 273 |
| IN1<8> | OUT<8>  | 13. 554 | IN1<10> | OUT<14> | 12. 713 |
| IN1<8> | OUT<9>  | 14. 571 | IN1<10> | OUT<15> | 14. 726 |
| IN1<8> | OUT<10> | 14. 012 | IN1<10> | OZF     | 16. 371 |
| IN1<8> | OUT<11> | 13. 549 | IN1<11> | OCF     | 13. 531 |
| IN1<8> | OUT<12> | 14. 619 | IN1<11> | ONF     | 14. 404 |
| IN1<8> | OUT<13> | 13. 720 | IN1<11> | OUT<0>  | 10. 740 |
| IN1<8> | OUT<14> | 13. 160 | IN1<11> | OUT<1>  | 10. 360 |
| IN1<8> | OUT<15> | 15. 173 | IN1<11> | OUT<2>  | 12. 755 |
| IN1<8> | OZF     | 16. 818 | IN1<11> | OUT<3>  | 10. 391 |
| IN1<9> | OCF     | 13. 483 | IN1<11> | OUT<4>  | 10. 991 |
| IN1<9> | ONF     | 14. 440 | IN1<11> | OUT<5>  | 11. 736 |
| IN1<9> | OUT<0>  | 10. 275 | IN1<11> | OUT<6>  | 12. 514 |
| IN1<9> | OUT<1>  | 10. 026 | IN1<11> | OUT<7>  | 11. 242 |
| IN1<9> | OUT<2>  | 12. 476 | IN1<11> | OUT<8>  | 11. 200 |
| IN1<9> | OUT<3>  | 10. 500 | IN1<11> | OUT<9>  | 11. 781 |
| IN1<9> | OUT<4>  | 10. 526 | IN1<11> | OUT<10> | 12. 062 |
| IN1<9> | OUT<5>  | 11. 402 | IN1<11> | OUT<11> | 13. 181 |
| IN1<9> | OUT<6>  | 12. 107 | IN1<11> | OUT<12> | 14. 383 |
| IN1<9> | OUT<7>  | 11. 651 | IN1<11> | OUT<13> | 13. 484 |
| IN1<9> | OUT<8>  | 10. 735 | IN1<11> | OUT<14> | 13. 060 |
| IN1<9> | OUT<9>  | 14. 304 | IN1<11> | OUT<15> | 14. 937 |
| IN1<9> | OUT<10> | 13. 945 | IN1<11> | OZF     | 16. 582 |
| IN1<9> | OUT<11> | 13. 883 | IN1<12> | OCF     | 12. 442 |
| IN1<9> | OUT<12> | 14. 448 | IN1<12> | ONF     | 14. 407 |
| IN1<9> | OUT<13> | 14. 148 | IN1<12> | OUT<0>  | 11. 332 |
| IN1<9> | OUT<14> | 13. 551 | IN1<12> | OUT<1>  | 9. 862  |
| IN1<9> | OUT<15> | 14. 973 | IN1<12> | OUT<2>  | 12. 125 |

|         |         |         |         |         |         |
|---------|---------|---------|---------|---------|---------|
| IN1<12> | OUT<3>  | 10. 271 | IN1<14> | OUT<9>  | 13. 484 |
| IN1<12> | OUT<4>  | 11. 503 | IN1<14> | OUT<10> | 10. 847 |
| IN1<12> | OUT<5>  | 11. 238 | IN1<14> | OUT<11> | 13. 331 |
| IN1<12> | OUT<6>  | 11. 884 | IN1<14> | OUT<12> | 12. 867 |
| IN1<12> | OUT<7>  | 11. 122 | IN1<14> | OUT<13> | 13. 881 |
| IN1<12> | OUT<8>  | 11. 748 | IN1<14> | OUT<14> | 12. 698 |
| IN1<12> | OUT<9>  | 11. 283 | IN1<14> | OUT<15> | 14. 711 |
| IN1<12> | OUT<10> | 11. 432 | IN1<14> | OZF     | 16. 356 |
| IN1<12> | OUT<11> | 12. 208 | IN1<15> | OCF     | 12. 956 |
| IN1<12> | OUT<12> | 14. 278 | IN1<15> | ONF     | 13. 269 |
| IN1<12> | OUT<13> | 13. 379 | IN1<15> | OUT<0>  | 11. 748 |
| IN1<12> | OUT<14> | 12. 927 | IN1<15> | OUT<1>  | 11. 608 |
| IN1<12> | OUT<15> | 14. 940 | IN1<15> | OUT<2>  | 10. 928 |
| IN1<12> | OZF     | 16. 585 | IN1<15> | OUT<3>  | 9. 855  |
| IN1<13> | OCF     | 12. 186 | IN1<15> | OUT<4>  | 11. 919 |
| IN1<13> | ONF     | 13. 957 | IN1<15> | OUT<5>  | 13. 382 |
| IN1<13> | OUT<0>  | 11. 236 | IN1<15> | OUT<6>  | 11. 022 |
| IN1<13> | OUT<1>  | 10. 941 | IN1<15> | OUT<7>  | 10. 521 |
| IN1<13> | OUT<2>  | 12. 293 | IN1<15> | OUT<8>  | 12. 164 |
| IN1<13> | OUT<3>  | 10. 401 | IN1<15> | OUT<9>  | 12. 467 |
| IN1<13> | OUT<4>  | 11. 407 | IN1<15> | OUT<10> | 11. 156 |
| IN1<13> | OUT<5>  | 12. 715 | IN1<15> | OUT<11> | 12. 971 |
| IN1<13> | OUT<6>  | 12. 052 | IN1<15> | OUT<12> | 12. 219 |
| IN1<13> | OUT<7>  | 11. 252 | IN1<15> | OUT<13> | 12. 864 |
| IN1<13> | OUT<8>  | 11. 652 | IN1<15> | OUT<14> | 12. 166 |
| IN1<13> | OUT<9>  | 11. 800 | IN1<15> | OUT<15> | 14. 486 |
| IN1<13> | OUT<10> | 11. 600 | IN1<15> | OZF     | 16. 131 |
| IN1<13> | OUT<11> | 12. 338 | IN2<0>  | OCF     | 12. 822 |
| IN1<13> | OUT<12> | 11. 707 | IN2<0>  | ONF     | 14. 238 |
| IN1<13> | OUT<13> | 12. 837 | IN2<0>  | OUT<0>  | 12. 933 |
| IN1<13> | OUT<14> | 12. 477 | IN2<0>  | OUT<1>  | 14. 335 |
| IN1<13> | OUT<15> | 14. 490 | IN2<0>  | OUT<2>  | 13. 305 |
| IN1<13> | OZF     | 16. 135 | IN2<0>  | OUT<3>  | 14. 806 |
| IN1<14> | OCF     | 13. 262 | IN2<0>  | OUT<4>  | 13. 895 |
| IN1<14> | ONF     | 14. 178 | IN2<0>  | OUT<5>  | 13. 974 |
| IN1<14> | OUT<0>  | 12. 396 | IN2<0>  | OUT<6>  | 13. 769 |
| IN1<14> | OUT<1>  | 12. 625 | IN2<0>  | OUT<7>  | 13. 414 |
| IN1<14> | OUT<2>  | 10. 619 | IN2<0>  | OUT<8>  | 13. 838 |
| IN1<14> | OUT<3>  | 11. 394 | IN2<0>  | OUT<9>  | 14. 867 |
| IN1<14> | OUT<4>  | 12. 567 | IN2<0>  | OUT<10> | 14. 091 |
| IN1<14> | OUT<5>  | 14. 399 | IN2<0>  | OUT<11> | 13. 624 |
| IN1<14> | OUT<6>  | 10. 713 | IN2<0>  | OUT<12> | 14. 456 |
| IN1<14> | OUT<7>  | 12. 245 | IN2<0>  | OUT<13> | 13. 571 |
| IN1<14> | OUT<8>  | 12. 812 | IN2<0>  | OUT<14> | 12. 890 |

|        |         |  |         |        |         |  |         |
|--------|---------|--|---------|--------|---------|--|---------|
| IN2<0> | OUT<15> |  | 14. 771 | IN2<3> | OUT<2>  |  | 10. 644 |
| IN2<0> | OZF     |  | 17. 313 | IN2<3> | OUT<3>  |  | 14. 175 |
| IN2<1> | OCF     |  | 12. 670 | IN2<3> | OUT<4>  |  | 13. 325 |
| IN2<1> | ONF     |  | 14. 069 | IN2<3> | OUT<5>  |  | 12. 835 |
| IN2<1> | OUT<0>  |  | 11. 390 | IN2<3> | OUT<6>  |  | 13. 496 |
| IN2<1> | OUT<1>  |  | 14. 107 | IN2<3> | OUT<7>  |  | 13. 141 |
| IN2<1> | OUT<2>  |  | 13. 077 | IN2<3> | OUT<8>  |  | 13. 588 |
| IN2<1> | OUT<3>  |  | 14. 578 | IN2<3> | OUT<9>  |  | 14. 617 |
| IN2<1> | OUT<4>  |  | 13. 667 | IN2<3> | OUT<10> |  | 13. 841 |
| IN2<1> | OUT<5>  |  | 13. 591 | IN2<3> | OUT<11> |  | 13. 374 |
| IN2<1> | OUT<6>  |  | 13. 541 | IN2<3> | OUT<12> |  | 14. 206 |
| IN2<1> | OUT<7>  |  | 13. 186 | IN2<3> | OUT<13> |  | 13. 321 |
| IN2<1> | OUT<8>  |  | 13. 610 | IN2<3> | OUT<14> |  | 12. 666 |
| IN2<1> | OUT<9>  |  | 14. 639 | IN2<3> | OUT<15> |  | 14. 669 |
| IN2<1> | OUT<10> |  | 13. 863 | IN2<3> | OZF     |  | 16. 682 |
| IN2<1> | OUT<11> |  | 13. 396 | IN2<4> | OCF     |  | 12. 475 |
| IN2<1> | OUT<12> |  | 14. 228 | IN2<4> | ONF     |  | 14. 059 |
| IN2<1> | OUT<13> |  | 13. 343 | IN2<4> | OUT<4>  |  | 13. 030 |
| IN2<1> | OUT<14> |  | 12. 589 | IN2<4> | OUT<5>  |  | 12. 529 |
| IN2<1> | OUT<15> |  | 14. 602 | IN2<4> | OUT<6>  |  | 13. 385 |
| IN2<1> | OZF     |  | 17. 085 | IN2<4> | OUT<7>  |  | 13. 030 |
| IN2<2> | OCF     |  | 14. 092 | IN2<4> | OUT<8>  |  | 13. 508 |
| IN2<2> | ONF     |  | 14. 503 | IN2<4> | OUT<9>  |  | 14. 537 |
| IN2<2> | OUT<0>  |  | 11. 317 | IN2<4> | OUT<10> |  | 13. 761 |
| IN2<2> | OUT<1>  |  | 10. 989 | IN2<4> | OUT<11> |  | 13. 294 |
| IN2<2> | OUT<2>  |  | 13. 121 | IN2<4> | OUT<12> |  | 14. 126 |
| IN2<2> | OUT<3>  |  | 14. 618 | IN2<4> | OUT<13> |  | 13. 241 |
| IN2<2> | OUT<4>  |  | 13. 711 | IN2<4> | OUT<14> |  | 12. 579 |
| IN2<2> | OUT<5>  |  | 13. 221 | IN2<4> | OUT<15> |  | 14. 592 |
| IN2<2> | OUT<6>  |  | 13. 863 | IN2<4> | OZF     |  | 16. 237 |
| IN2<2> | OUT<7>  |  | 13. 508 | IN2<5> | OCF     |  | 12. 572 |
| IN2<2> | OUT<8>  |  | 13. 955 | IN2<5> | ONF     |  | 13. 617 |
| IN2<2> | OUT<9>  |  | 14. 984 | IN2<5> | OUT<5>  |  | 12. 020 |
| IN2<2> | OUT<10> |  | 14. 208 | IN2<5> | OUT<6>  |  | 12. 944 |
| IN2<2> | OUT<11> |  | 13. 741 | IN2<5> | OUT<7>  |  | 12. 589 |
| IN2<2> | OUT<12> |  | 14. 573 | IN2<5> | OUT<8>  |  | 13. 067 |
| IN2<2> | OUT<13> |  | 13. 688 | IN2<5> | OUT<9>  |  | 14. 096 |
| IN2<2> | OUT<14> |  | 13. 023 | IN2<5> | OUT<10> |  | 13. 320 |
| IN2<2> | OUT<15> |  | 15. 036 | IN2<5> | OUT<11> |  | 12. 972 |
| IN2<2> | OZF     |  | 17. 125 | IN2<5> | OUT<12> |  | 13. 685 |
| IN2<3> | OCF     |  | 13. 589 | IN2<5> | OUT<13> |  | 13. 237 |
| IN2<3> | ONF     |  | 14. 136 | IN2<5> | OUT<14> |  | 12. 640 |
| IN2<3> | OUT<0>  |  | 11. 656 | IN2<5> | OUT<15> |  | 14. 150 |
| IN2<3> | OUT<1>  |  | 10. 763 | IN2<5> | OZF     |  | 15. 795 |

|        |         |  |         |         |         |  |         |
|--------|---------|--|---------|---------|---------|--|---------|
| IN2<6> | OCF     |  | 12. 778 | IN2<9>  | OUT<15> |  | 13. 987 |
| IN2<6> | ONF     |  | 13. 438 | IN2<9>  | OZF     |  | 15. 632 |
| IN2<6> | OUT<6>  |  | 12. 744 | IN2<10> | OCF     |  | 12. 684 |
| IN2<6> | OUT<7>  |  | 12. 389 | IN2<10> | ONF     |  | 13. 769 |
| IN2<6> | OUT<8>  |  | 12. 860 | IN2<10> | OUT<10> |  | 12. 988 |
| IN2<6> | OUT<9>  |  | 13. 889 | IN2<10> | OUT<11> |  | 12. 680 |
| IN2<6> | OUT<10> |  | 13. 240 | IN2<10> | OUT<12> |  | 13. 748 |
| IN2<6> | OUT<11> |  | 13. 178 | IN2<10> | OUT<13> |  | 13. 113 |
| IN2<6> | OUT<12> |  | 13. 743 | IN2<10> | OUT<14> |  | 12. 733 |
| IN2<6> | OUT<13> |  | 13. 443 | IN2<10> | OUT<15> |  | 14. 302 |
| IN2<6> | OUT<14> |  | 12. 846 | IN2<10> | OZF     |  | 15. 947 |
| IN2<6> | OUT<15> |  | 13. 971 | IN2<11> | OCF     |  | 12. 784 |
| IN2<6> | OZF     |  | 15. 616 | IN2<11> | ONF     |  | 14. 021 |
| IN2<7> | OCF     |  | 12. 296 | IN2<11> | OUT<11> |  | 12. 798 |
| IN2<7> | ONF     |  | 13. 301 | IN2<11> | OUT<12> |  | 14. 000 |
| IN2<7> | OUT<7>  |  | 12. 211 | IN2<11> | OUT<13> |  | 13. 213 |
| IN2<7> | OUT<8>  |  | 12. 711 | IN2<11> | OUT<14> |  | 12. 833 |
| IN2<7> | OUT<9>  |  | 13. 740 | IN2<11> | OUT<15> |  | 14. 554 |
| IN2<7> | OUT<10> |  | 12. 964 | IN2<11> | OZF     |  | 16. 199 |
| IN2<7> | OUT<11> |  | 12. 696 | IN2<12> | OCF     |  | 12. 268 |
| IN2<7> | OUT<12> |  | 13. 329 | IN2<12> | ONF     |  | 14. 255 |
| IN2<7> | OUT<13> |  | 12. 961 | IN2<12> | OUT<12> |  | 14. 126 |
| IN2<7> | OUT<14> |  | 12. 364 | IN2<12> | OUT<13> |  | 13. 227 |
| IN2<7> | OUT<15> |  | 13. 834 | IN2<12> | OUT<14> |  | 12. 775 |
| IN2<7> | OZF     |  | 15. 479 | IN2<12> | OUT<15> |  | 14. 788 |
| IN2<8> | OCF     |  | 12. 707 | IN2<12> | OZF     |  | 16. 433 |
| IN2<8> | ONF     |  | 14. 222 | IN2<13> | OCF     |  | 12. 260 |
| IN2<8> | OUT<8>  |  | 13. 136 | IN2<13> | ONF     |  | 14. 031 |
| IN2<8> | OUT<9>  |  | 14. 153 | IN2<13> | OUT<13> |  | 12. 911 |
| IN2<8> | OUT<10> |  | 13. 594 | IN2<13> | OUT<14> |  | 12. 551 |
| IN2<8> | OUT<11> |  | 13. 131 | IN2<13> | OUT<15> |  | 14. 564 |
| IN2<8> | OUT<12> |  | 14. 201 | IN2<13> | OZF     |  | 16. 209 |
| IN2<8> | OUT<13> |  | 13. 372 | IN2<14> | OCF     |  | 13. 025 |
| IN2<8> | OUT<14> |  | 12. 775 | IN2<14> | ONF     |  | 13. 316 |
| IN2<8> | OUT<15> |  | 14. 755 | IN2<14> | OUT<14> |  | 13. 074 |
| IN2<8> | OZF     |  | 16. 400 | IN2<14> | OUT<15> |  | 14. 001 |
| IN2<9> | OCF     |  | 12. 281 | IN2<14> | OZF     |  | 15. 646 |
| IN2<9> | ONF     |  | 13. 454 | IN2<15> | OCF     |  | 11. 763 |
| IN2<9> | OUT<9>  |  | 13. 318 | IN2<15> | ONF     |  | 12. 406 |
| IN2<9> | OUT<10> |  | 12. 759 | IN2<15> | OUT<15> |  | 12. 939 |
| IN2<9> | OUT<11> |  | 12. 681 | IN2<15> | OZF     |  | 14. 584 |
| IN2<9> | OUT<12> |  | 13. 433 | OPC<0>  | OCF     |  | 9. 503  |
| IN2<9> | OUT<13> |  | 12. 946 | OPC<0>  | ONF     |  | 11. 649 |
| IN2<9> | OUT<14> |  | 12. 349 | OPC<0>  | OUT<0>  |  | 12. 029 |

|        |         |  |         |                    |         |  |         |
|--------|---------|--|---------|--------------------|---------|--|---------|
| OPC<0> | OUT<1>  |  | 12. 216 | OPC<2>             | OUT<1>  |  | 11. 251 |
| OPC<0> | OUT<2>  |  | 10. 337 | OPC<2>             | OUT<2>  |  | 9. 446  |
| OPC<0> | OUT<3>  |  | 12. 646 | OPC<2>             | OUT<3>  |  | 10. 876 |
| OPC<0> | OUT<4>  |  | 11. 584 | OPC<2>             | OUT<4>  |  | 10. 257 |
| OPC<0> | OUT<5>  |  | 11. 515 | OPC<2>             | OUT<5>  |  | 10. 084 |
| OPC<0> | OUT<6>  |  | 10. 763 | OPC<2>             | OUT<6>  |  | 10. 141 |
| OPC<0> | OUT<7>  |  | 11. 660 | OPC<2>             | OUT<7>  |  | 9. 871  |
| OPC<0> | OUT<8>  |  | 11. 829 | OPC<2>             | OUT<8>  |  | 10. 647 |
| OPC<0> | OUT<9>  |  | 13. 034 | OPC<2>             | OUT<9>  |  | 10. 700 |
| OPC<0> | OUT<10> |  | 11. 819 | OPC<2>             | OUT<10> |  | 10. 016 |
| OPC<0> | OUT<11> |  | 11. 438 | OPC<2>             | OUT<11> |  | 10. 664 |
| OPC<0> | OUT<12> |  | 12. 263 | OPC<2>             | OUT<12> |  | 10. 740 |
| OPC<0> | OUT<13> |  | 12. 201 | OPC<2>             | OUT<13> |  | 10. 889 |
| OPC<0> | OUT<14> |  | 11. 425 | OPC<2>             | OUT<14> |  | 10. 415 |
| OPC<0> | OUT<15> |  | 12. 182 | OPC<2>             | OUT<15> |  | 10. 503 |
| OPC<0> | OZF     |  | 15. 153 | OPC<2>             | OZF     |  | 13. 383 |
| OPC<1> | OCF     |  | 13. 487 | OPC<3>             | OCF     |  | 9. 336  |
| OPC<1> | ONF     |  | 12. 225 | OPC<3>             | ONF     |  | 9. 819  |
| OPC<1> | OUT<0>  |  | 11. 984 | OPC<3>             | OUT<0>  |  | 10. 068 |
| OPC<1> | OUT<1>  |  | 12. 323 | OPC<3>             | OUT<1>  |  | 10. 900 |
| OPC<1> | OUT<2>  |  | 10. 400 | OPC<3>             | OUT<2>  |  | 9. 095  |
| OPC<1> | OUT<3>  |  | 12. 641 | OPC<3>             | OUT<3>  |  | 10. 525 |
| OPC<1> | OUT<4>  |  | 12. 219 | OPC<3>             | OUT<4>  |  | 10. 517 |
| OPC<1> | OUT<5>  |  | 12. 441 | OPC<3>             | OUT<5>  |  | 9. 733  |
| OPC<1> | OUT<6>  |  | 11. 027 | OPC<3>             | OUT<6>  |  | 9. 790  |
| OPC<1> | OUT<7>  |  | 12. 249 | OPC<3>             | OUT<7>  |  | 9. 520  |
| OPC<1> | OUT<8>  |  | 12. 984 | OPC<3>             | OUT<8>  |  | 10. 296 |
| OPC<1> | OUT<9>  |  | 13. 360 | OPC<3>             | OUT<9>  |  | 10. 349 |
| OPC<1> | OUT<10> |  | 11. 422 | OPC<3>             | OUT<10> |  | 9. 665  |
| OPC<1> | OUT<11> |  | 12. 633 | OPC<3>             | OUT<11> |  | 10. 313 |
| OPC<1> | OUT<12> |  | 13. 329 | OPC<3>             | OUT<12> |  | 10. 389 |
| OPC<1> | OUT<13> |  | 12. 638 | OPC<3>             | OUT<13> |  | 10. 538 |
| OPC<1> | OUT<14> |  | 11. 714 | OPC<3>             | OUT<14> |  | 10. 127 |
| OPC<1> | OUT<15> |  | 12. 758 | OPC<3>             | OUT<15> |  | 10. 215 |
| OPC<1> | OZF     |  | 15. 148 | OPC<3>             | OZF     |  | 13. 032 |
| OPC<2> | OCF     |  | 9. 922  | -----+-----+-----+ |         |  |         |
| OPC<2> | ONF     |  | 9. 648  |                    |         |  |         |
| OPC<2> | OUT<0>  |  | 10. 419 |                    |         |  |         |

## Appendix 5: RTL Diagram of ALU Pipeline Example

